


Q1) Write Verilog code to describe the following functions

$$f1 = ac' + bc + b'c'$$

$$f2 = (a + b' + c)(a + b + c')(a' + b + c')$$

Ans 1) Part 1)

```
module q1a(a, b, c, f);  
  
    input a, b, c;  
  
    output f;  
  
    // creating compliments  
    // not(b_, b);  
    // not(c_, c);  
  
    // getting and gates  
    and(x1, a, ~c);  
    and(x2, b, c);  
    and(x3, ~b, ~c);  
    or(f, x1, x2, x3);  
endmodule
```

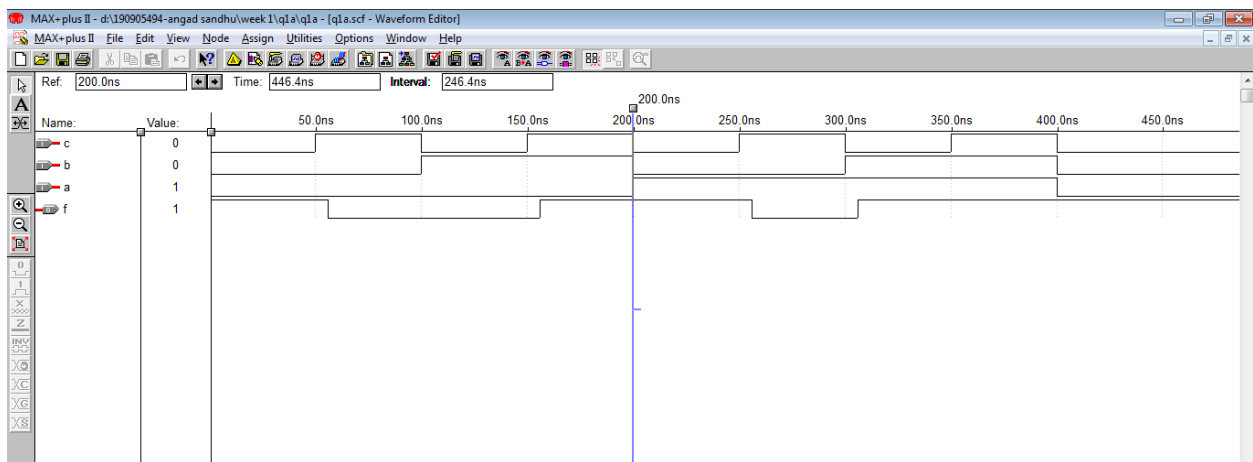

Ans 1) Part 2)

```
module q1b(a, b, c, f);
```

```
    input a, b, c;
```

```
    output f;
```

```
// getting and gates
```


```
or(x1, a, ~b, c);
```

```
or(x2, a, b, ~c);
```

```
or(x3, ~a, b, ~c);
```

```
and(f, x1, x2, x3);
```

```
endmodule
```

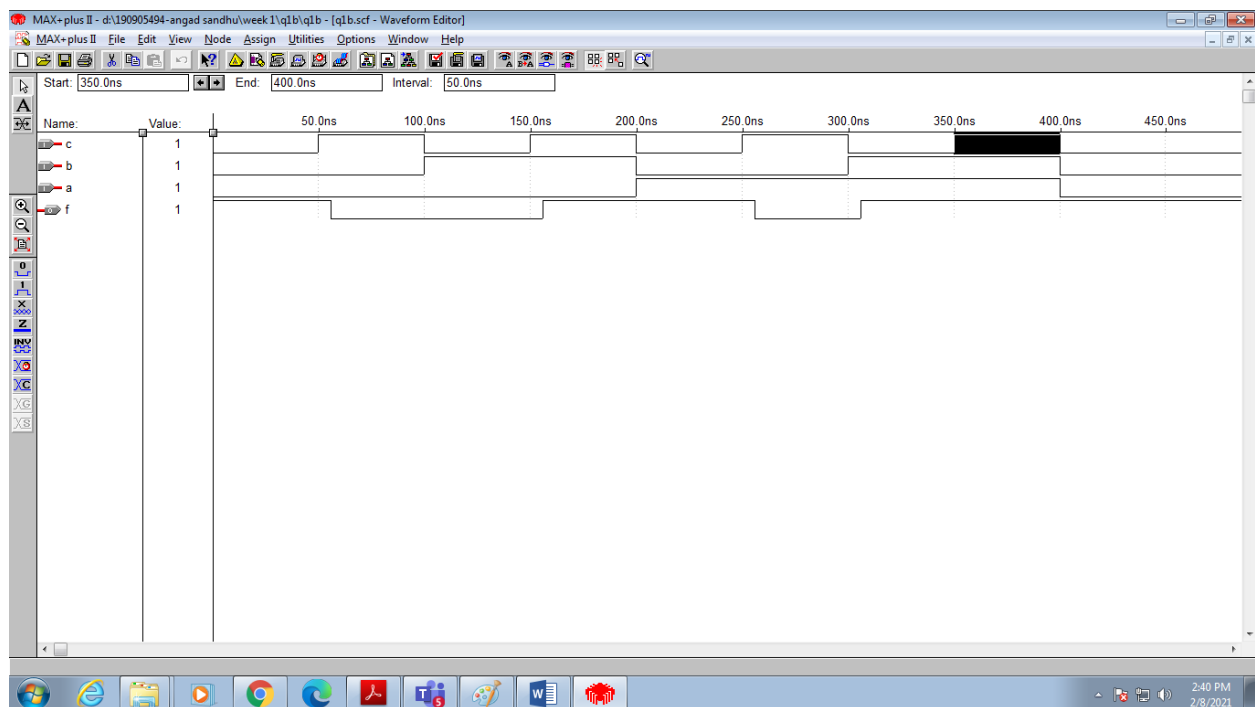

Q2) Part 1)

// equation to be minimized :

// $f(A, B, C, D) = \sum m(1, 3, 4, 9, 10, 12) + D(0, 2, 5, 11)$

// the minimized term of the equation :

// $\text{Ans} = B'D + B'C + BC'D'$

// using continuous assignment statements


module q2a(a, b, c, d, f);

input a, b, c, d;

output f;

assign f = ($\sim b \& d$) | ($\sim b \& c$) | ($b \& \sim c \& \sim d$);

endmodule

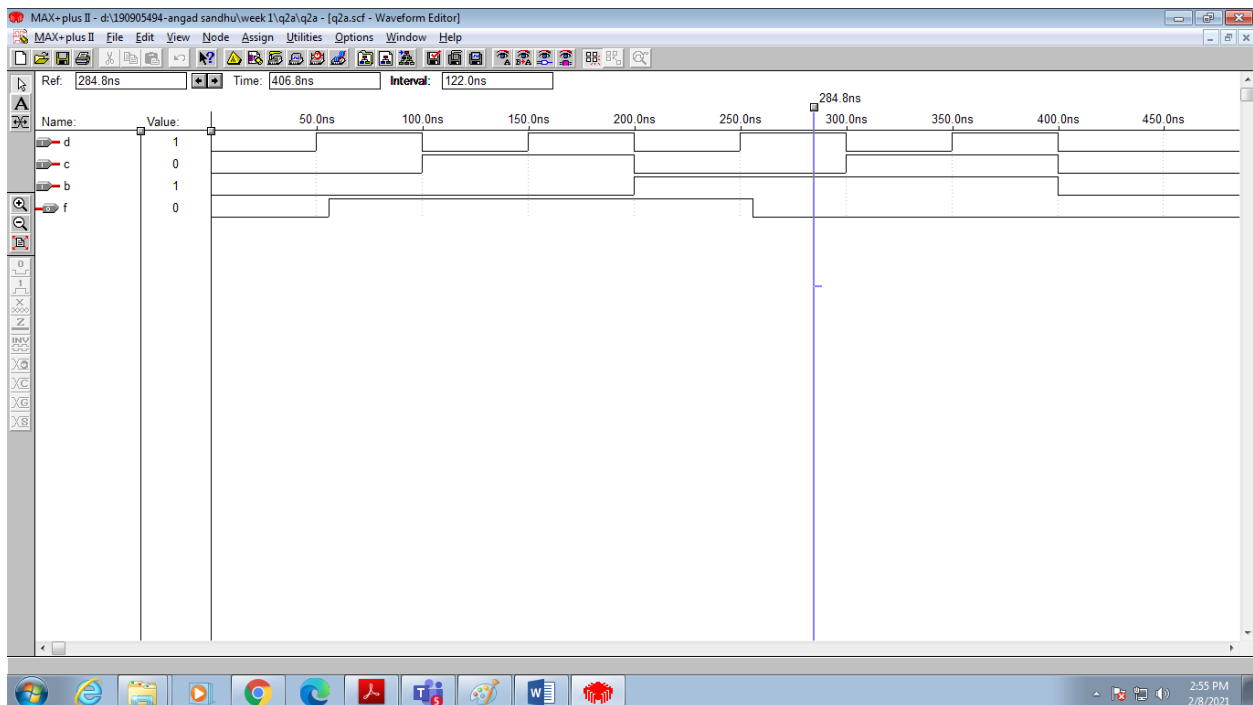

Q2) part 2)

// equation to be minimized:

// $f(A, B, C, D) = \sum m(6, 9, 10, 11, 12) + \sum d(2, 4, 7, 13)$

// the minimized term of the equation:

// $\text{Ans} = B'C'D' + ABC + A'D$

// using continuous assignment statements


module q2b(a, b, c, d, f);

input a, b, c, d;

output f;

assign f = (~a & d) | (~b & ~c & ~d) | (a & b & c);

endmodule

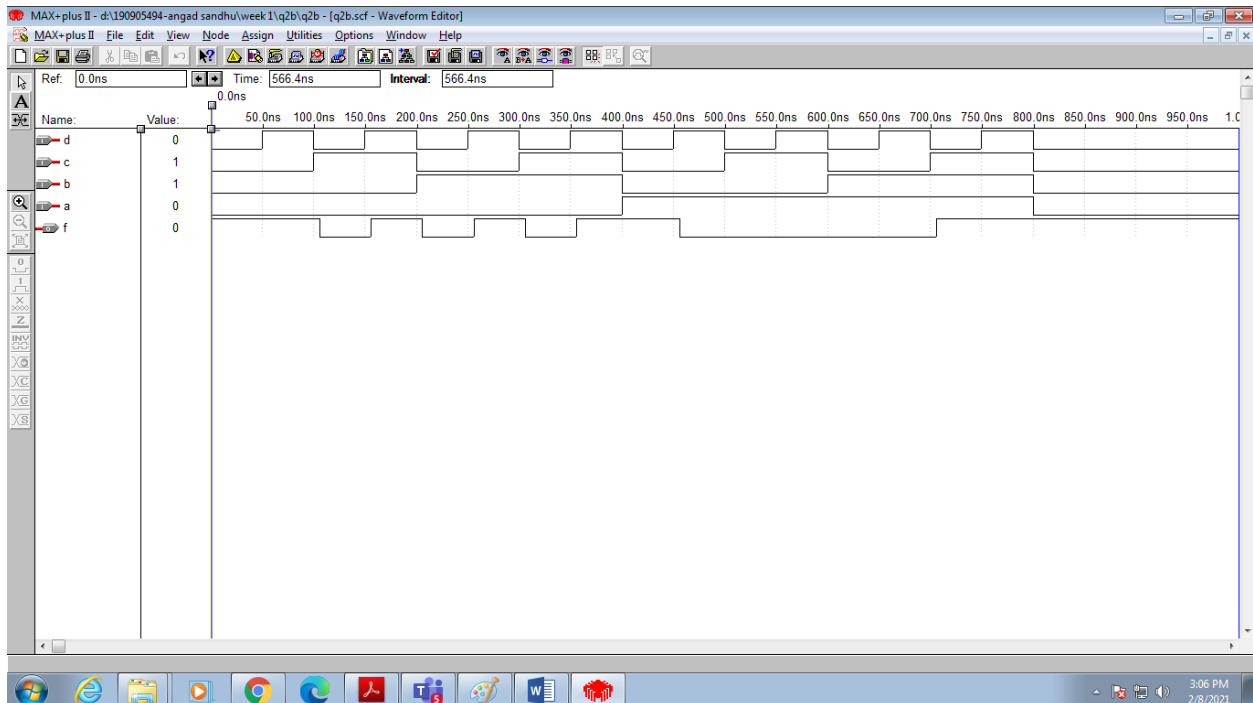

Q3)

// equation to be minimized :

// $f(A, B, C, D) = \sum m(2, 6, 8, 9, 10, 11, 14)$

// the minimized term of the equation :

// $Ans = A'C' + A'D + BC' + BD$

// using continuous assignment statements

module q3(a, b, c, d, f);

input a, b, c, d;

output f;

nand(x1, ~a, ~c);

nand(x2, ~a, d);

nand(x3, b, ~c);

nand(x4, b, d);

nand(f, x1, x2, x3, x4);

endmodule

